

ID										Name:
----	--	--	--	--	--	--	--	--	--	-------

Post-Lab Questions (2 marks in total, 2/3 marks for each question):

- (1) By examining your plots on Graph (1.3), answer the following:
 - a) What are the effects of the dc-supply voltages on the voltage-transfer characteristics?
 - b) Would the solo Op-amp qualify as a practical amplifier circuit? Comment on your answer.

- (2) By considering your plots on Graphs (1.3), (1.4) & (1.5), answer the following:
 - a) What does the application of negative feedback (around the Op-amp) have on the amplifier-circuit behavior?
 - b) Does the application of negative feedback have any effect on the output saturation voltages? Comment on your answer.

- (3) By comparing the results of your investigation of the inverting and non-inverting configurations, answer the following:
 - a) What is the most desirable feature of the inverting configuration, and what is its weakest characteristic?
 - b) What is the most desirable characteristic of the non-inverting configuration?
 - c) What is that desirable feature that both configurations enjoy relative to no Op-Amp circuits? [Hint: Think about the effects of connecting circuits in cascade.]