# Experiment #4 Introduction to Digital Multimeters, Oscilloscopes & Function Generators

#### 4.1 Introduction:

At each station in our electric-circuits laboratories a standard set of instruments is available to enable you to conduct your investigations of circuit behaviour. These instruments are capable of providing the following:

- a) Generate test signals such as sinusoidal, triangular, and square waveforms with adjustable amplitude and frequency. These signals can be level-shifted [up or down] with the addition of a dc-offset component,
- b) Measure dc and/or ac voltage & current, resistance, and frequency, and
- c) Display voltage waveforms on a CRT.

This experiment introduces these instruments and demonstrates their capabilities and limitations.


#### 4.2 Prelab Assignment:

Read the Appendix-section associated with this experiment and familiarize yourself with the various controls of each instrument.
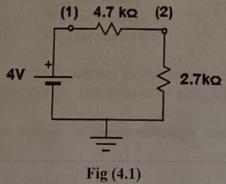
#### 4.3 Procedure:

1- Connect the dc-circuit shown in Fig (4.1). Set the oscilloscope controls as follows: Signal Coupling (<u>CHx MENU</u>→<u>Coupling</u>) dc, Y-Position (VERTICAL <u>POSITION</u> knobs) screen centre, and Vertical Sensitivity (<u>VOLTS/DIV</u> knobs) 1V/div for both channels "1" & "2".

Connect channels "1" & "2" to display the voltage waveforms @ nodes (1) & (2) respectively.



2- Use the oscilloscope to measure the voltages @ nodes (1) & (2).

$$V_{(1)} = 4.000 V$$
 &  $V_{(2)} = 1.459 V$ 

3- Use the DMM to measure the voltages @ nodes (1) & (2).

$$V_{(1)}=$$
 4 V &  $V_{(2)}=$  1.459 V

4- With the oscilloscope connected as in step #1, set the following additional controls as: Horizontal Sensitivity (SEC/DIV knob) • 0.2 msec/div, Trigger Source (TRIG  $\underline{MENU} \rightarrow \underline{Source}$ )  $\blacktriangleleft$  CH1, and Trigger Slope (TRIG MENU $\rightarrow \underline{Slope}$ )  $\blacktriangleleft$  Rising.

Replace the dc-source in the circuit of Fig (4.1) with the function generator. Set the controls of the function generator to provide a sinusoidal voltage of 2V (peak) with a frequency of about 1kHz @ node (1).

Use the DMM to measure the voltage & frequency [using the dual display of the DMM] of the signal @ node (1). Adjust the frequency of the function generator to exactly 1kHz.

[DMM readings: Frequency = 
$$10^3$$
 Hz &  $V_{(1)} = 4.702$  V.]

5- Set the "waveform-select" control of the function generator to square wave, and use the DMM to measure the voltage & frequency @ node (1).

[DMM readings: Frequency = 
$$[0]^3$$
 Hz &  $V_{(1)} = 8_{1000}$  V.]

6- Set the waveform-select control of the function generator to triangular wave, and use the DMM to measure the voltage & frequency @ node (1).

[DMM readings: Frequency = 
$$10^3$$
 Hz &  $V_{(1)} = 2$ , 9/9 V.]

7- Use the "dc-offset" control of the function generator to provide a triangular wave of 4V (peak-to-peak) with an average value of 2V at a frequency of 1kHz @ node (1). Note that the amplitude of the waveform is now fluctuating in the voltage range: 0.0V to 4V @ 1kHz. Use the DMM to measure each of the following voltage entities @ node (1):

a) The dc-component.....  $V_{(1)}$  [dc-value] = 1.532 V, b) The ac-component.....  $V_{(1)}$  [ac-value] = 2.578 V, and c) The [ac + dc]-value...  $V_{(1)}$  [ac+dc-value] = 2.999 V.

8- Set the controls of the function generator [with the help of the oscilloscope] to provide a sinusoidal signal of 20mV (peak) with an average value of 2V at a frequency of 1kHz @ node (1).

Note that the present settings of the oscilloscope controls will not enable you to perform the above step !!}

[Hint: Use the dc/ac-coupling & Vertical (Voltage) Sensitivity controls of Channel "1" to separately set accurately the dc & ac components of the desired signal]

Use the DMM to measure the dc & ac components of the voltage @ node (1), and record your measurements in table (4.1).

9- Set the "frequency" control of function generator to each of the values listed in table (4.1), and repeat the above step.

Table (4.1) [DMM measurements]


Frequency (kHz)	DC Component (V)	AC Component (mV)
1.0	2	14.9
10.0	1.515	14.97
100.0	1,514	14,559
1000.0	1,510	14.507

10-Connect the circuit shown in Fig (4.2). Connect channels "1" & "2" of the oscilloscope to node (1) & (2), respectively. Note Channel 2 will now display a scaled-up version of the current =  $(10,000) \times i$  (t). Set the oscilloscope controls as follows:

Signal Coupling (<u>CHx MENU → Coupling</u>) • ac, Y-Position (VERTICAL <u>POSITION</u> knobs) • screen centre, and Vertical Sensitivity (<u>VOLTS/DIV</u> knobs) • 1V/div for both channels "1" & "2", Horizontal Sensitivity (<u>SEC/DIV</u> knob) • 0.1 msec/div, Trigger Source (<u>TRIG MENU → Source</u>) • CH1, and Trigger Slope (<u>TRIG MENU → Slope</u>) • Rising.

Set the controls of the function generator to provide a sinusoidal voltage of 4V (peak) with a frequency of about 1kHz @ node (1).

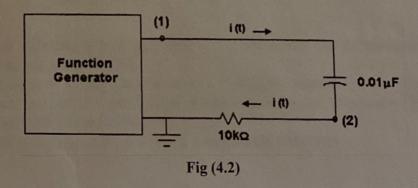Note the displays of the waveforms of  $V_{(1)}(t)$  and i(t) are both sinusoids with the same frequency, but with a different magnitude and phase angle.



11-Use the oscilloscope to measure the phase angle  $(\theta^{\circ})$  of i(t) relative to  $V_{(1)}(t)$ . This measurement can be performed in **one-out-of-two** ways depending on the mode of operation of the oscilloscope [(Y-Time) or (X-Y) mode]:

#### **Phase Measurement**

### A) With The Oscilloscope In The Y-Time Display Mode:

Proceed by setting the oscilloscope controls as follows:

First: Set the Y-Position (VERTICAL <u>POSITION</u> knobs) for both "1" & "2" screen centre, and Horizontal Sensitivity (<u>SEC/DIV</u> knob) to display about one period of the Channel 1 display. Adjust Trigger Level (<u>LEVEL</u> knob) to trigger the Channel 1 display @ the positive-going zero crossing instant, and move this point (with X-Position (HORIZONTAL <u>POSITION</u> knob) adjustment) to the left end of the display.

Second: Using Horizontal Controls (<u>HORIZ MENU</u>→<u>Window Zone</u>) to set one-half period of the Channel 1 display to occupy <u>exactly nine divisions</u> along the x-axis.

[The x-axis is now calibrated for phase-angle measurements with a scale of 20% div.]

Measure the phase angle ( $\theta^{\circ}$ ) and record your result in table (4.2).

## B) With The Oscilloscope In The X-Y Display Mode:

Proceed by setting the oscilloscope controls as follows:

Set Display Format (<u>DISPLAY</u> → <u>Format</u>) of the oscilloscope to XY mode. Note that the oscilloscope is now using the signal from Channel 1 to control the X coordinate and the signal from Channel 2 to control the Y coordinate. The oscilloscope is now operating in the X-Y display mode.

The vertical deflection is now controlled by the current i(t), and the horizontal deflection is controlled by the voltage  $V_{(1)}(t)$ .

Generally, the X-Y display [usually called a "Lissajous pattern"] is an ellipse; the ratio of [its intersection with the Y-axis  $(y_0)$ ]-to-[its maximum vertical deflection  $(y_m)$ ] is used to find the phase angle  $(\theta^o)$  as indicated in Fig (4.3).

Measure the phase angle  $(\theta^{\circ})$  and record your result in table (4.2)

(Table 4.2) [Phase angle ( $\theta^{\circ}$ ) of i(t) wrt  $V_{(1)}(t)$ ]

Y-Time-display mode	X-Y-dispaly mode

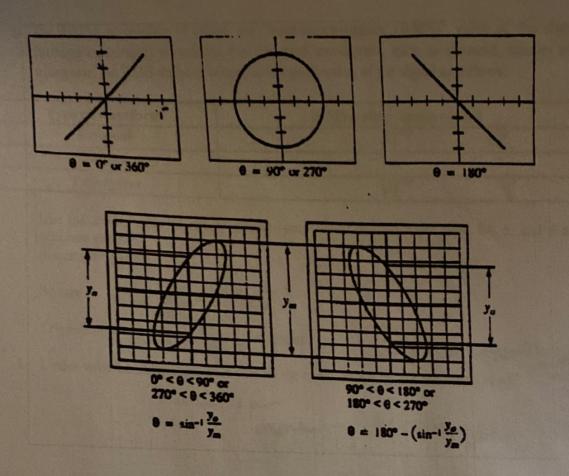


Fig (4.3)

#### 4.4 Conclusion:

1- Compare your measurements from steps #2 & 3. Which set of measurements would you consider to be more accurate, and why?

both gave me exact same value so both are equally accurate

2- The DMM ac-reading is called the "root-mean-square (RMS)" value of the signal (voltage or current) waveform. For standard waveforms, such as sinusoid, square, and triangular, the RMS-value is related to the peak-value of the signal as follows:

Type of waveform	[RMS-value] /[peak-value]
Sinusoid	[2]-0.5
Square	1 1
Triangular	[3]-0.5

Use the above table to check whether your measurements from steps #4, 5, and 6 are

Sinusoid: 4702

Square: 4.702 x \( \frac{3}{3} = 2.714 \)

Triangular: 4.702 x \( \frac{3}{3} = 2.714 \)

3- Under which conditions would you set the oscilloscope coupling-control to \( \frac{ac}{ac} \)?

activities

when I am measuring the voltage

4- Discuss the results of your measurements listed in table (4.1).

Frequency has little to no change one The Ac and DC Valves

5- In comparing the two methods of phase measurement [step #11], which one do you think is more accurate, and why?