

lab 1

Fig (1.1a)


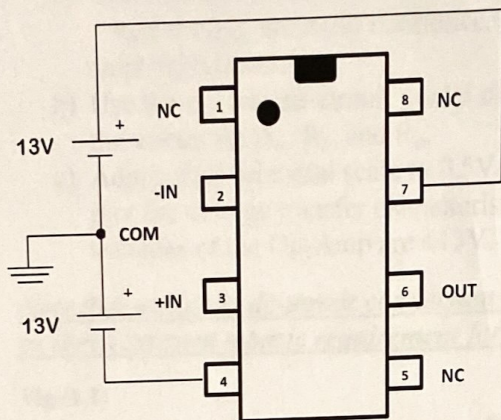



Fig (1.1b)

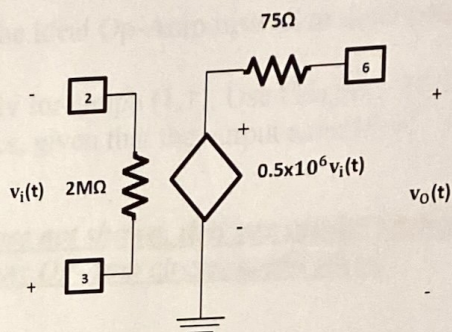

### 1.3 Prelab Assignment (3 marks in total, 1 mark for each step):

**Step 1:** The circuit in Fig (1.1a) shows the pin identification for the  $\mu A741$  Op-Amp and the connections of the two dc-power supplies that are required for its operation. Suppose now that pin (2) is connected to the common ground (COM), while a triangular wave, voltage  $v_i(t)$ , is applied to pin (3), use Graph (1.1) to show how the resulting voltage-transfer characteristics,  $[v_o(t) \text{ vs } v_i(t)]$ , would look like, given that the output saturation voltages of the Op-Amp are  $\pm 13\text{V}$  and the equivalent-circuit model of the Op-Amp is shown in Fig (1.1b).


Graph (1.1)

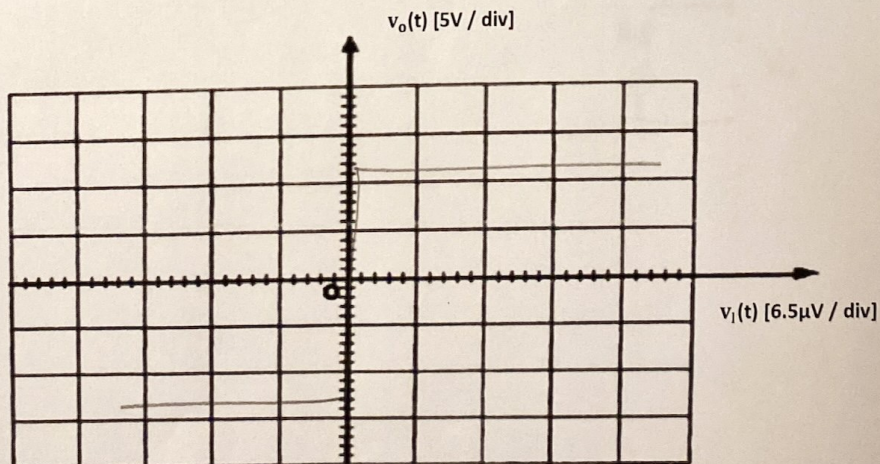


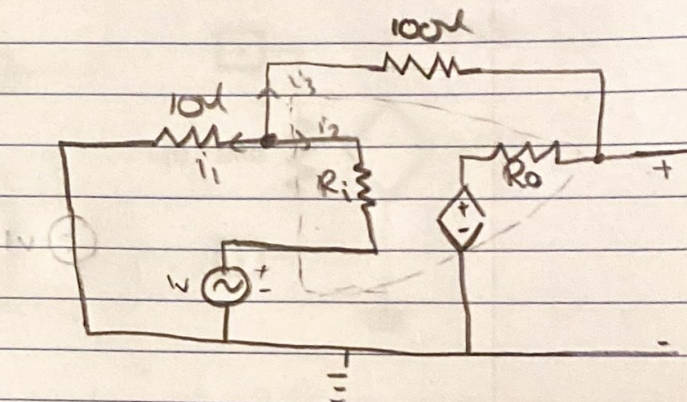
# pre lab 1


2a)  $V_1 = 1$   
 $V_0 = ?$   
 $R_0 = ?$   
 $R_i = ?$



$$0 + \frac{0-1}{R_i} + \frac{0-V_0}{100k} = 0$$

$$\frac{-1}{R_i} = \frac{V_0}{100k\Omega} \quad \text{only 1 node!}$$

$R_i = 2M\Omega$   
 $R_0 = 75\Omega$

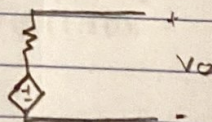

3) a)

$$\frac{0-1}{10k} + \frac{0-V_0}{100k} = 0$$

$$\frac{V_0}{100} = \frac{1}{10k}$$

$$\boxed{V_0 = 10V}$$

$A = \frac{10}{1} \quad \boxed{A = 10}$

