

$$1) a) V_{Th} = I_C \left[R + \frac{1}{\omega C} \right]$$

$$Z = R - \frac{1}{\omega C}$$

$$|Z| = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$$

$$|Z| = \sqrt{(3.9k)^2 + \left(\frac{1}{2000\pi \times 10^{-8}} \right)^2}$$

$$|Z| = 16.39 k\Omega$$

$$\theta = \arctan \left(\frac{1}{2000\pi \times 10^{-8}} \right) = 78.63^\circ$$

$$I_C = \frac{A}{Z} = \frac{5}{16.4} = 0.304 \angle 78.63^\circ$$

b)

$$Z = \sqrt{(5.9)^2 + \left(\frac{1}{\omega C} \right)^2}$$

$$I_C = \frac{5}{Z}$$

$$\theta = \arctan \left(\frac{1}{\omega C} \right)$$

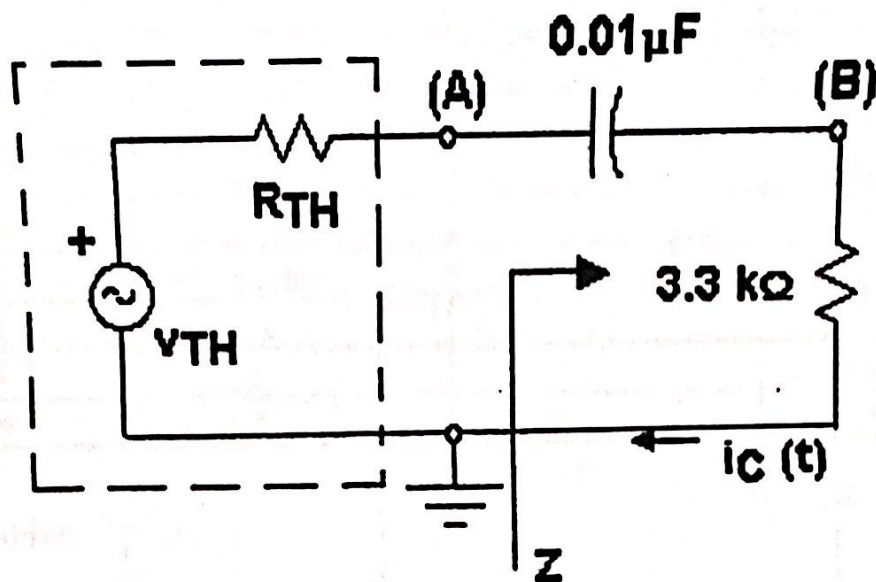


Fig (6.1)

Table (6.1)

Frequency (kHz)	$ Z $ (k Ω)	θ°_Z	$ I_C $ (mA)
0.5	32.855	83	0.155
1	16.4	78	0.3
2	8.86	63.75	0.59
5	5.032	39.5	0.95
10	4.21	22	1.186
20	3.98	11.5	1.25
50	3.92	4.66	1.277

- 2- Suppose that the capacitor in Fig (6.1) is replaced with a “practical” inductor whose equivalent circuit consists of a series combination of an inductive element of **0.5H** and a resistive element of **700 Ω** .
- Find the **SSS expression** for the inductor current $i_L(t)$.
 - Suppose that the frequency of $v_{TH}(t)$ is varied as listed in table (6.2), find the magnitude and phase angle of the impedance Z , where $Z = |Z| \angle \theta^\circ_Z$, and the peak value of the inductor current $|I_L|$, for each frequency setting.

Table (6.2)

Frequency (kHz)	$ Z $ (k Ω)	θ°_Z	$ I_L $ (mA)
0.1	4.012	4.48	1.23
0.2	4.05	8.92	1.25
0.5	4.297	21.4	1.16
1	5.085	38.13	0.98
2	7.45	57.5	0.67
5	16.20	75.7	0.308
10	31.65	82.7	0.159

6.4 Procedure:

Part I: The Sinusoidal-Steady-State Behaviour of An RC Circuit

- 1- Connect channel "1" of the oscilloscope across the output terminals of the function generator. Set the controls of the function generator to provide an "open-circuit" sinusoidal voltage of 5V (peak) @ a frequency (f) of 500Hz.

Connect the circuit shown in Fig (6.1). Set the oscilloscope for **ac-coupling, Y-Positions @ screen centre, Trigger Source @ Channel 1, and Trigger Slope @ Rising**. Connect channel "1" of the oscilloscope to display the voltage waveform @ node (A), and channel "2" to display the voltage waveform @ node (B). [The "2" display now represents the (scaled-up) current waveform (3300) $i_C(t)$.]

- 2- Measure the peak-value of $v_A(t)$ and $v_B(t)$, and record in table (6.3) under $|V_A|$ & $|V_B|$, respectively. Evaluate the peak value of the current $|I_C|$.

Phase-Angle Measurement

To measure the phase angle θ° [which is defined here as the phase angle of $v_B(t)$ relative to $v_A(t)$] as accurately as possible, proceed by setting the oscilloscope controls as follows:

First: Set **Horizontal Sensitivity** to display about **one period** of the "1" display. Adjust **Trigger Level** to trigger the "1" display @ the positive-going **zero crossing** instant, and move this point (with "X-Position" adjustment) to the left end of the screen.