

Lab#5 Pulse Response of Simple RC & RL Circuits

This lab demonstrates the **transient response** of the capacitor and inductor. The voltage of the capacitor gradually **changes up**, as the current of the inductor gradually charges up with the following differential equations:

Capacitor	Inductor
$i_C(t) = C \frac{dv_C}{dt}$	$v_L(t) = L \frac{di_L}{dt}$

The voltage across the capacitor of a simple RC circuit in Fig. (5.1) can be expressed as:

$$v_C(t > 0) = V_{ss} + (V_{0-} - V_{ss})e^{-\frac{t}{\tau}}, \text{ where } \tau = R_{total}C \text{ and } V_{ss} = V_T$$

Since $V_0 = 0V$,

$$v_C(t > 0) = V_{ss}(1 - e^{-\frac{t}{\tau}}) \quad (1)$$

The current through the inductor of a simple RL circuit in Fig. (5.2) can be expressed as:

$$i_L(t > 0) = I_{ss} + (I_{0-} - I_{ss})e^{-\frac{t}{\tau}}, \text{ where } \tau = L/R_{total} \text{ and } I_{ss} = \frac{V_T}{R_{total}}$$

Since $I_0 = 0 \text{ A}$,

$$i_L(t > 0) = I_{ss}(1 - e^{-\frac{t}{\tau}}) \quad (2)$$

The characteristics of the capacitor and inductor at transient $t=0^+$ are as follows:

	Capacitor	Inductor
Current	Max	Charging
Voltage	Charging	Max

The initial values of the voltage and current at $t=0^+$ can be obtained by replacing $t=0$ in equations (1) and (2), and their differential equations:

Multisim

Please follow the steps below to setup the simulation environment and build your circuits


1. Setting up **Interactive simulation** environment
2. Use the following components to build your circuits:
 - Resistor: RESISTOR_RATED
 - Capacitor: CAPACITOR_RATED
 - Inductor: INDUCTOR_RATED
3. You only need to use:
 - Function generator as voltage source
 - Oscilloscope to measure voltage signal

Lab Procedure


Part I. Internal resistance of the function generator

A physical function generator has a Thevenin equivalent internal resistance. In the lab manual, this internal resistance is given as $R_T=600\Omega$. Multisim function generator does not have an internal resistance. You will need to add a resistor to learn how to measure the internal resistance.

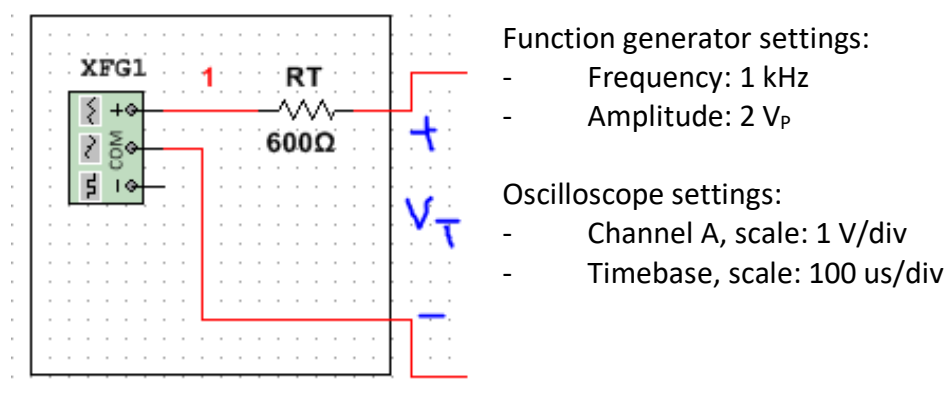Step 1: Connect a 600Ω resistor to the function generator to act as R_T . Set the function generator as described in the lab manual and use an oscilloscope (Channel A) to measure the open circuit voltage V_T .



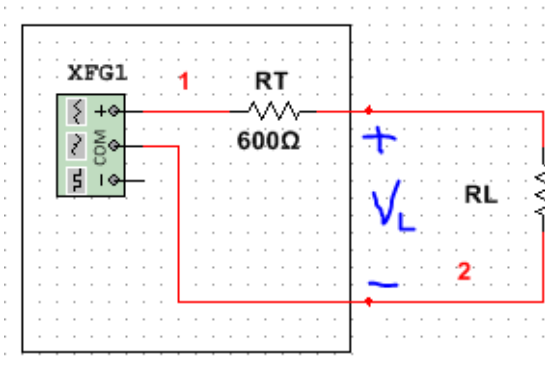Step 2: Connect a load resistor and measure the voltage. You will find R_T , when $V_L = \frac{V_T}{2}$




Step 3: Change the V_T to a different waveform and V_{peak} . You will still get $V_L = \frac{V_T}{2}$ when $R_L = R_T$.

Part II: The RC-circuit pulse response

NOTE: Switching Steps 4 and 5 from the lab manual

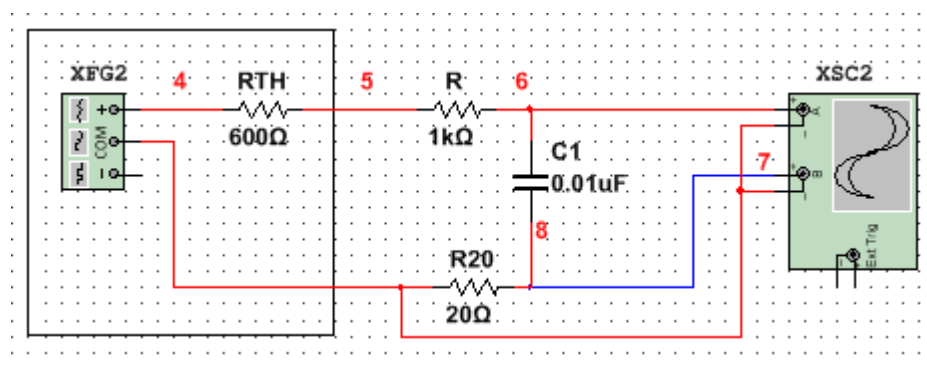Step 4: Construct the circuit with Channel A measuring the capacitor voltage and Channel B measuring the capacitor current. The capacitor current is the same as the current through 20Ω resistor, $i_C(t) = \frac{v_{R20}}{20}$.



Step 5: Set the function generator to provide a square wave at 1 kHz frequency with 3 V_P AC and 3V DC offset:

- Waveforms: Square wave
- Frequency: 1 kHz
- Amplitude: 3 VP
- Offset: 3V

Use default oscilloscope settings with the following changes:

Timebase	Channel A	Channel B	Trigger
Scale: 100 μ s/Div	Scale: 1 V/Div Y pos. (Div): -3	Scale: 50 mV/Div	Use Auto. But, try Single to display 1 duty cycle.

NOTE: Make sure you can see the rising edge of the capacitor voltage.

Step 6: Plot $v_C(t)$ and $i_C(t)$ using Graphs (5.1) and (5.2), respectively. Beam off Channel B to plot $v_C(t)$, by pressing the 0 button. Then, beam off Channel A to plot $i_C(t)$.


Step 7: Measure τ using the capacitor voltage. Beam off Channel B.

At steady state, when $t = \infty$,

$$v_C(t = 0) = V_{ss}(1 - e^{-\infty}) = V_T(1 - 0) = V_T$$

When $t = \tau$,

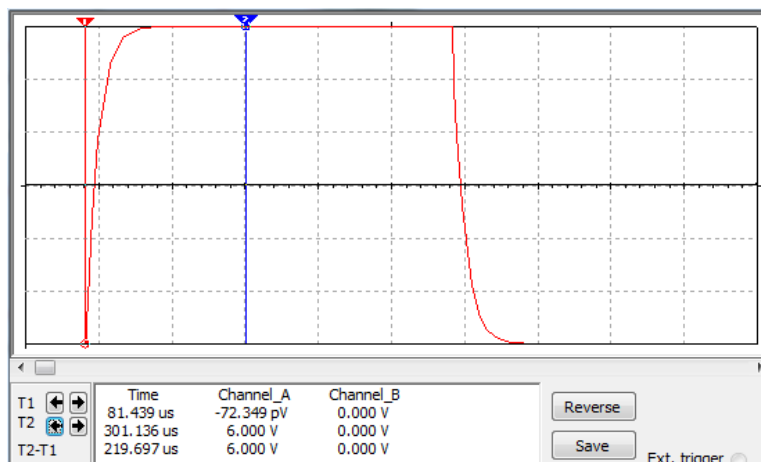
$$v_C(t = \tau) = V_{ss}(1 - e^{-\frac{\tau}{\tau}}) = V_T(1 - 0.37) = 0.63V_T$$



Place T1 at the beginning of the transient

Use T2 to measure V_T ($V_T = 6$ V)

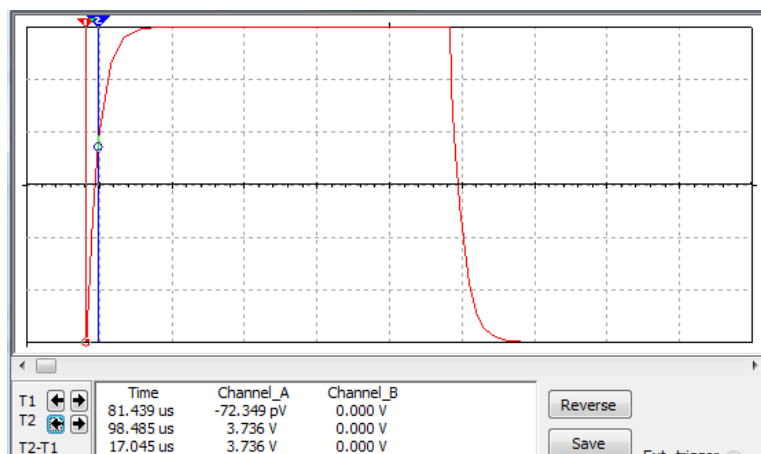That means when $t = \tau$,
 $v_C(t) = 3.79$ V



Move T2 to channel A voltage as close to 3.79 V as possible.

The time constant for the capacitor voltage to change up to $v_C = 3.79$ V is:

$$T2 - T1 = 17 \mu\text{s}$$

Step 8: Replace the 1 k Ω with R=6.8 k Ω and plot the graphs. If you cannot see the signals on the oscilloscope, make sure you change the Trigger setting back to Auto.

Part II: The RL-Circuit Pulse Response

Step 9: Build the circuit by replacing the capacitor with an L=50 mH inductor and set R back to 1 k Ω .

Change the oscilloscope settings to:

Timebase	Channel A	Channel B	Trigger
Scale: 100 μ s/Div	Scale: 2 V/Div Y pos. (Div): -2	Scale: 20 mV/Div Y pos. (Div): -2	Use Auto. But, try Single to display 1 duty cycle.

Plot the $i_L(t)$ and $v_L(t)$ in Graphs (5.3) and (5.4), respectively

Repeat the measurement for time constant τ and max. inductor voltage (v_L) in Table 5.6.

From equation (2), the voltage across the inductor is


$$v_L(t) = L \frac{di_L}{dt} = I_{ss} \frac{L}{\tau} e^{-\frac{t}{\tau}} = K e^{-\frac{t}{\tau}}$$

When $t = 0$, voltage across the inductor is maximum,

$$v_L(t = 0) = K e^{-\frac{0}{\tau}} = K$$

When $t = \tau$,
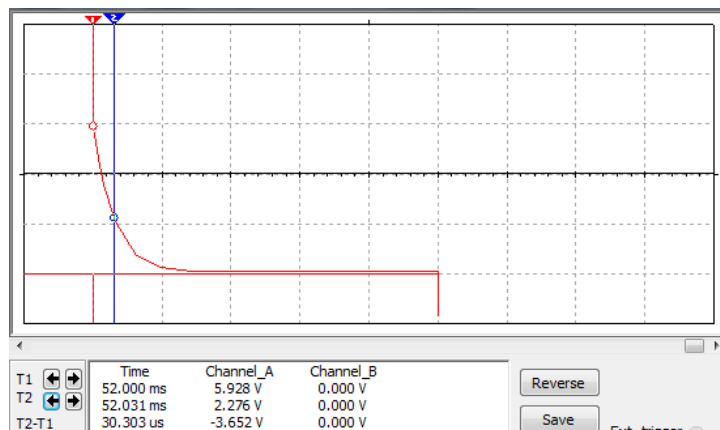
$$v_L(t = \tau) = K e^{-\frac{\tau}{\tau}} = 0.37 K$$



Use T1 to measure K at $t = 0$. K should be close to V_T .

Since $K=5.928$,

$$v_L(t = \tau) = 2.19 V$$

Move T2 to as close to 2.19 as possible to get

$$\tau = T2 - T1 = 30 \mu s$$

Repeat the step using L=150 mH.