

Conclusion

5-)

with inductors

Voltage controls current

with capacitors

Current controls voltage

6) Shorting The capacitor/inductor
To fix it Subtract channel 2 from
Channel 1