

# Pre-Lab1

Sunday, January 17, 2021 7:16 PM

AHMAD EL-GOHARY 501011852

## 1.3 Prelab Assignment:



- Use Graph (1.1) to plot the  $i$ - $v$  characteristic of a  $3.3 \text{ k}\Omega$  resistor, and a  $10 \text{ k}\Omega$  resistor.
- Use your plots to find the missing data in the following table.

Resistor	Voltage across (V)	Current through (mA)	Power absorbed (mW)
$3.3 \text{ k}\Omega$	10	3	30
$10 \text{ k}\Omega$	10		10
$3.3 \text{ k}\Omega$	3.3	1	3.3
$10 \text{ k}\Omega$	10	1	10

1




1 a),b)

$3.3 \text{ k}\Omega$

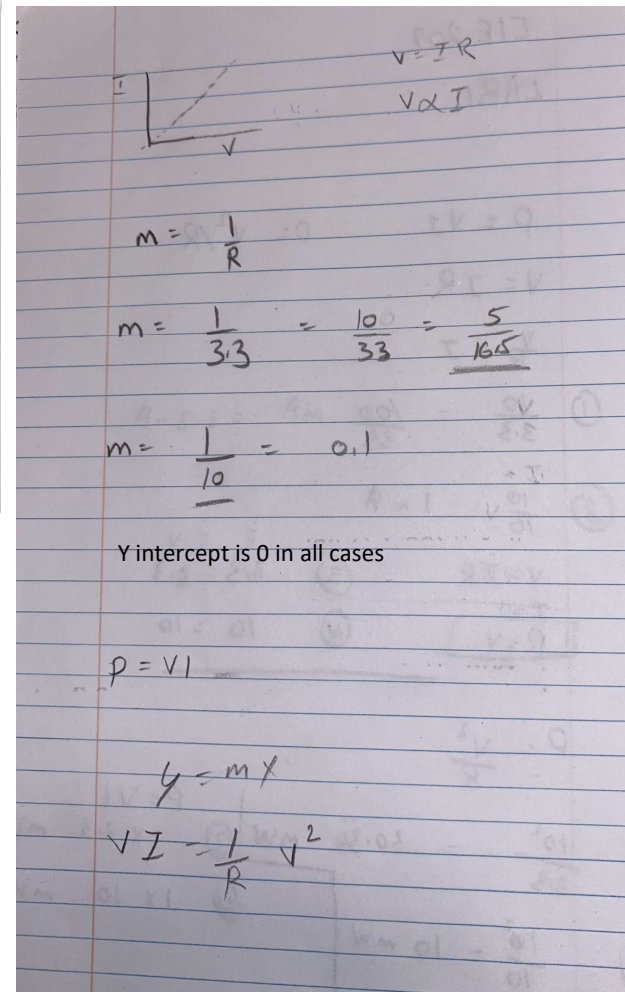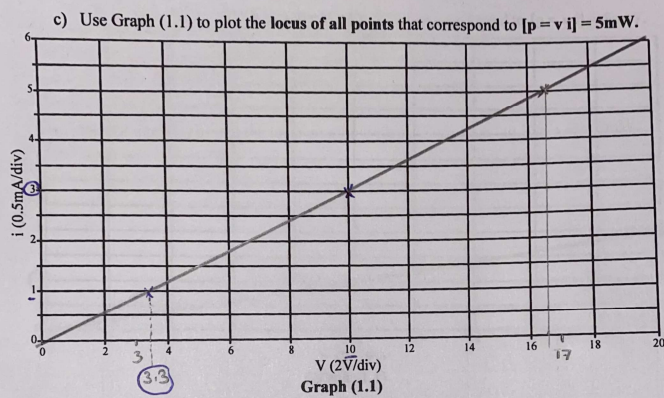


$$P=5 \quad I \cdot V=5$$

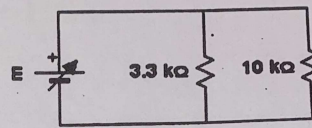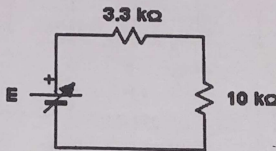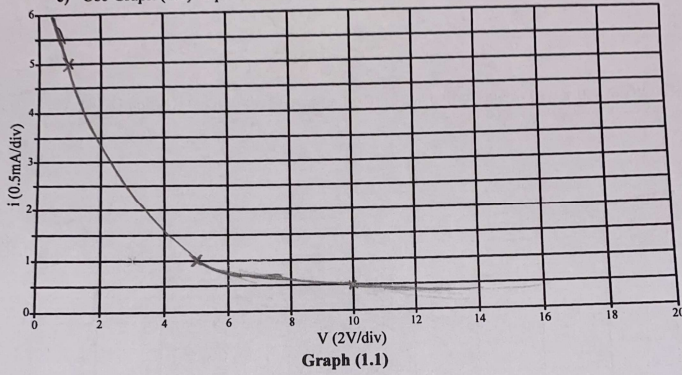c) Use Graph (1.1) to plot the locus of all points that correspond to  $[p = v i] = 5mW$ .



- 2- Consider the simple series circuit shown in Fig (1.1).
  - a) Find the value of the voltage source "E" that is required to provide a 10V across the 10kΩ resistor. What are the values of  $[V_{10k}/E]$  and  $[V_{3.3k}/V_{10k}]$ ?
  - b) Determine the amount of power supplied by the voltage source when  $E = 20V$ . What are the values of  $[P_{3.3k}/P_{10k}]$  and  $[P_{3.3k}/P_{supply}]$ ?
- 3- Consider the simple parallel circuit shown in Fig (1.2).
  - a) Find the value of "E" that is required to provide a 2mA current through the 10kΩ resistor. What are the values of  $[I_{3.3k}/I_{10k}]$  and  $[I_{3.3k}/I_{supply}]$ ?
  - b) Determine the amount of power supplied by the voltage source when the voltage across the 3.3 kΩ resistor is 10V. What are the values of  $[P_{3.3k}/P_{10k}]$  and  $[P_{3.3k}/P_{supply}]$ ?

2

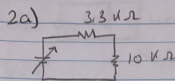

$$V = 10V$$

$$R = 10k\Omega$$

$$I = ?$$

$$V = IR$$

$$10 = I \cdot 10 \times 10^3$$

$$I = 0.001 \text{ Amps}$$

$$V = ?$$

$$R = 3300$$

$$I = 0.001$$

$$V = IR$$

$$V = 3300 \times 0.001$$

$$V = 3.3V$$

$$E = V_1 + V_2 = 13.3V$$

$$\frac{V_{10k}}{E} = \frac{10}{13.3}$$

$$\frac{V_{3.3k}}{V_{10k}} = \frac{3.3}{10}$$

$$2b) \quad V = 20$$

$$I = ?$$

$$R = 13.3k\Omega$$

$$\frac{V}{R} = I$$


$$I = 1.5038 \text{ mA}$$

$$P_{supply} = 20 \times 1.5038 \times 10^{-3} = 0.030075 \text{ W}$$

$$P_{3.3k} = I^2 R = \left(\frac{200}{133}\right)^2 \times 3.3 = 0.00746 \text{ W}$$

$$P_{10k} = I^2 R = \left(\frac{200}{133}\right)^2 \times 10 = 0.0226 \text{ W}$$

$\frac{P_{3.3k}}{P_{10k}} = \frac{7.46}{22.61}$	$\frac{P_{3.3k}}{P_{supply}} = \frac{7.46}{30}$
$= 0.3299$	$= 0.2487$

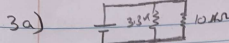

$$V = ?$$

$$I = 0.002$$

$$R = 10000$$

$$V = IR = 0.002 \times 10000 = 20$$

$$E = 20$$

$$V = 20$$

$$R = 3300$$

$$I = ?$$

$$\frac{V}{R} = I$$

$$I = 0.006061$$

$$\frac{I_{3.3k}}{I_{10k}} = \frac{0.006061}{0.002} = 3.03$$

$$\frac{I_{3.3k}}{I_T} = \frac{0.006061}{0.008061} = 0.752$$

$$3b) \quad V = 10$$

$$I = ?$$

$$R = 3300$$

$$V = IR$$

$$I = 0.00303$$

$$P_{3.3k} = 0.0305$$

$$P_{10k} = 0.01$$

$$\frac{P_{3.3k}}{P_{10k}} = \frac{0.0305}{0.01} = 3.03$$

$$V = 10$$

$$I = ?$$

$$R = 10000$$

$$I = 0.001$$

$$\frac{P_{3.3k}}{P_T} = \frac{0.0305}{0.0403} = 0.752$$