

Lab#3 Thevenin's Equivalent Circuit & Maximum Power Transfer

It is possible to replace a complicated circuit by a simple Thevenin's equivalent circuit consisting of a voltage source V_{TH} in series with a resistor R_{TH} . The maximum power transfer of 50% occurs when the load resistor R_L is equal to R_{TH} . The efficiency of power transfer $[\eta\%]$ is the percentage of source power transfer to the load, as provided in the manual

$$\eta \% = \frac{P_L}{P_S} \times 100\%$$

, where $P_L = V_L I_L$ is the power transferred to the load and $P_S = V_S I_S$ is the source power

Multisim

Please follow the steps below to setup the simulation environment and build your circuits

1. Setting up Interactive simulation environment
2. Place component on the circuit board to build your circuit

Repeat the steps above to place all components for your circuits

Circuit	Devices	Power	GROUND (Reference Node)
Fig (3.1)	3 RESISTOR_RATED 1 VARIABLE_RESISTOR - Resistor (R): 30 kΩ , - Increment: 1%	DC_POWER	1 optional
Thevenin's Equivalent	1 RESISTOR_RATED 1 VARIABLE_RESISTOR	DC_POWER	1 optional
Part II Thevenin's Equivalent	Change VARIABLE RESISTOR setting to: - Resistor (R): 340 kΩ , - Increment: 0.1%	DC_POWER	1 optional





Note: You cannot search for the VARIABLE_RESISTOR, but you can find it if you scroll down in the Family window.

3. You only need to use multimeters to measure the current and voltage.

Lab Procedure

Part I. Thevenin's equivalent circuit

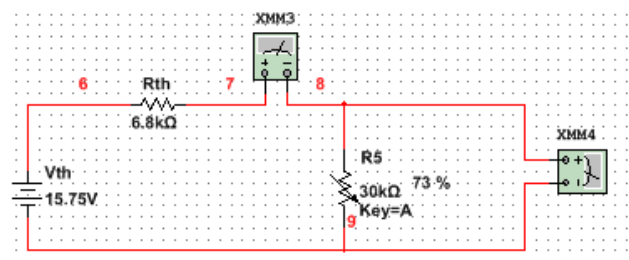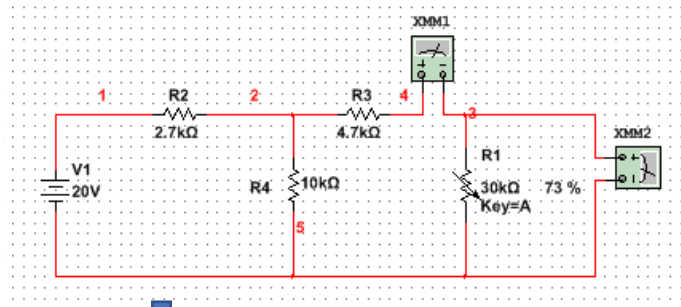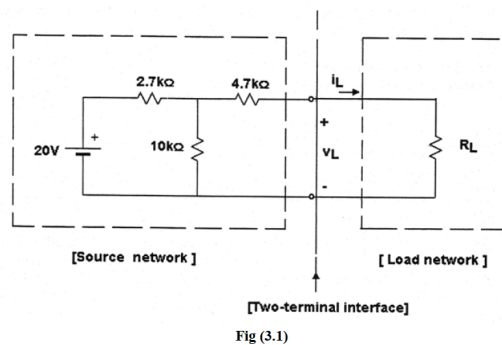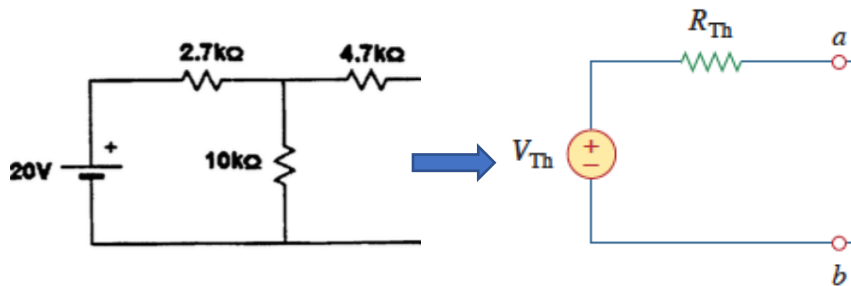1. Finding the Thevenin's equivalent circuit for the 2-terminal source network:



Thevenin's Equivalent

Part II. Power Transfer

Using the same Thevenin circuit with a different load resistor setting to complete Table 3.3, using $R_{TH} = 6.8 \text{ k}\Omega$.

Hint:

- Calculate R_L first for each column before measurement. E.g. $R_L/R_{TH} = 0.05 \Rightarrow R_L = 340 \Omega$
- Source power can be calculated as $P_S = (R_{TH} + R_L) I_L^2$